

Diodes

Simple two-terminal electronic devices.

Made of semiconducting materials: silicon, gallium arsenide, indium phosphide, gallium nitride, etc. (EE 332 stuff.)

Semiconductors are interesting because their electrical properties can be varied over many order of magnitude: resistivity as high as $10^7 \Omega\text{-m}$ (almost an insulator) or as low as $10^{-6} \Omega\text{-m}$ (almost a conductor).

Also, semiconductors can be made in two different “varieties”: either *n-type* in which current is carried by electrons (as usual) or *p-type* which current is carried by positive charges called holes.

A diode consists of a p-type layer of semiconductor joined to a n-type layer, and so is also known as a *p-n junction*. Current flowing across this junction exhibits a very asymmetric, non-linear i-v characteristic.

The non-linearity will force us to change the way we analyze circuits.

Diode applications

- Rectification – cutting off the top half or bottom half of a voltage signal.
- Voltage regulation – providing a steady voltage reference in a circuit.
- light-emitting diodes – for indicators
- light-emitting diodes – for illumination
- lasers - DVD players, fiber-optic communication, surgery
- photodetectors – sense presence of light, especially low levels or fast pulses
- photovoltaics (solar cells) – “green” electrical power generation
- building block for transistors




rectifying diode
(switching or *small-signal*)

made of silicon



LEDs – various materials (not silicon).
Different material = different colors.

laser



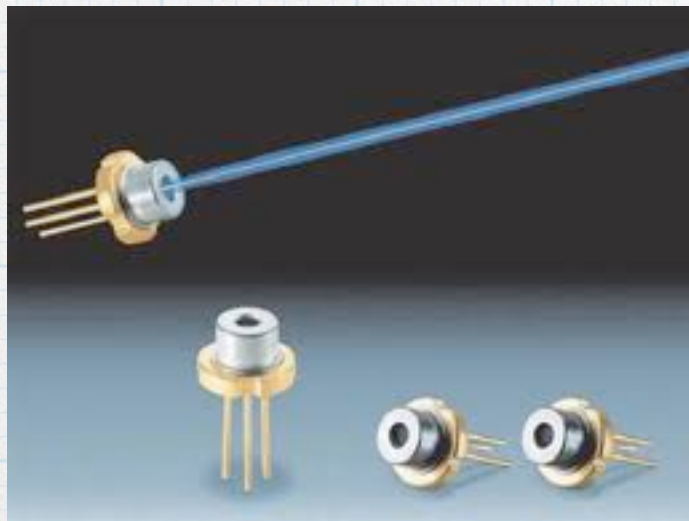


solar cell



LED lighting – usually gallium nitride
(UV light) that excites a phosphor.

Diode

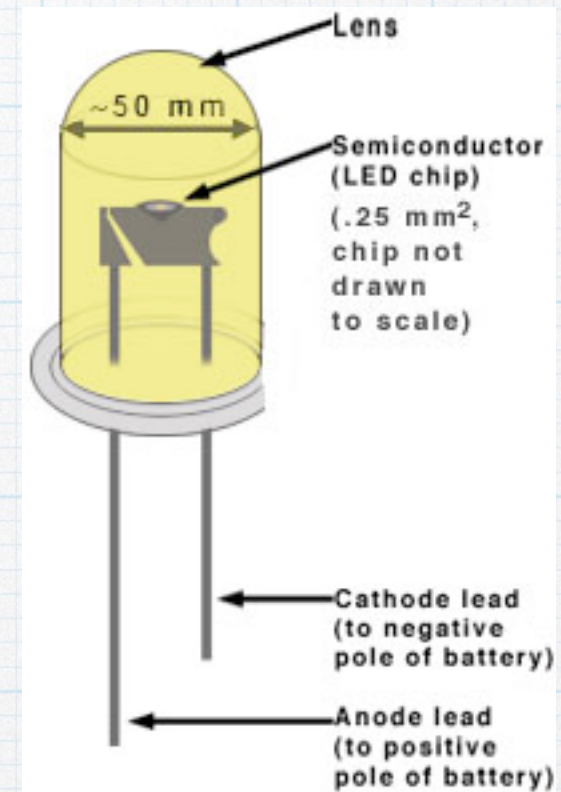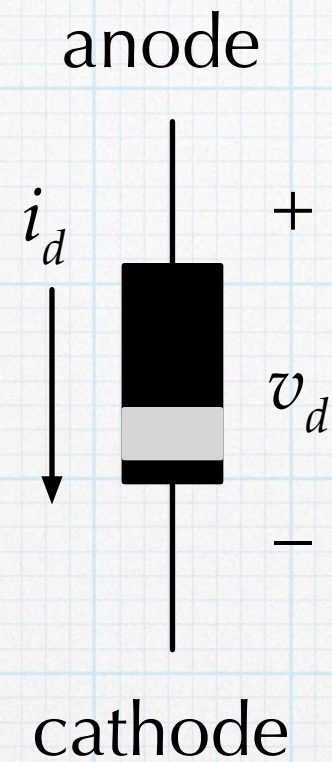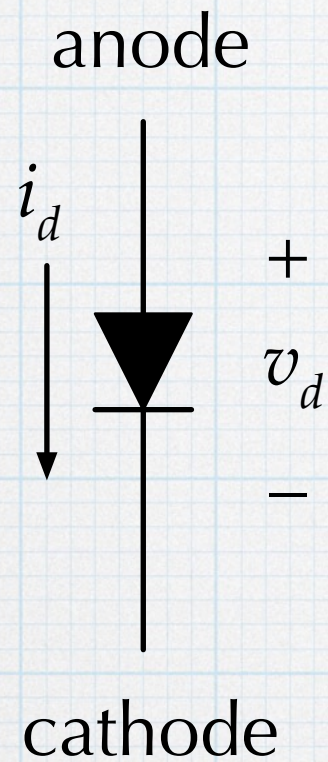


think “funnel” – it flows in one direction

diode i-v characteristic

ideal diode equation
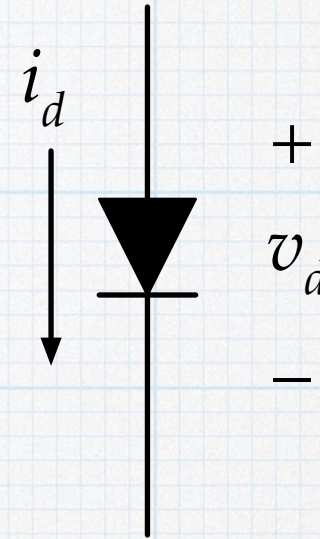
$$i_D = I_S \left[\exp \left(\frac{v_D}{kT/q} \right) - 1 \right]$$



Extremely non-linear. Will cause lots of problems in analyzing, but offers many opportunities for applications.

I_S is a parameter of the diode, known as *saturation current* or *scale current*. Different for every diode. (Like R for a resistor.)

Typical: $I_S \approx 10^{-14}$ A.


kT is the thermal energy. k (Boltzmann's constant = 1.38×10^{-23} J/K), T = temperature in kelvin (K).

q is the charge on one electron; kT/q is the thermal voltage.

At 300K (= 27°C, approximately room temperature), $kT/q = 25.8$ mV.

diode: forward and reverse conduction
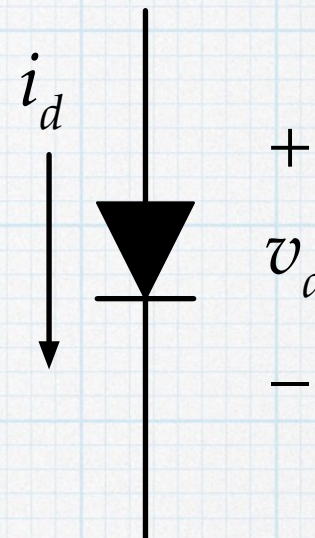
$$i_D = I_S \left[\exp \left(\frac{v_D}{kT/q} \right) - 1 \right]$$



If v_D is positive, $v_D \gg kT/q$.

$$i_D \approx I_S \exp \left(\frac{v_D}{kT/q} \right)$$



Lots of current can flow. Increases rapidly as v_D increases. Forward *bias* or forward conduction.

If v_D is negative.

$$i_D \approx -I_S$$

A very small trickle of current flows, almost zero. Independent of the voltage. Reverse bias or reverse conduction.

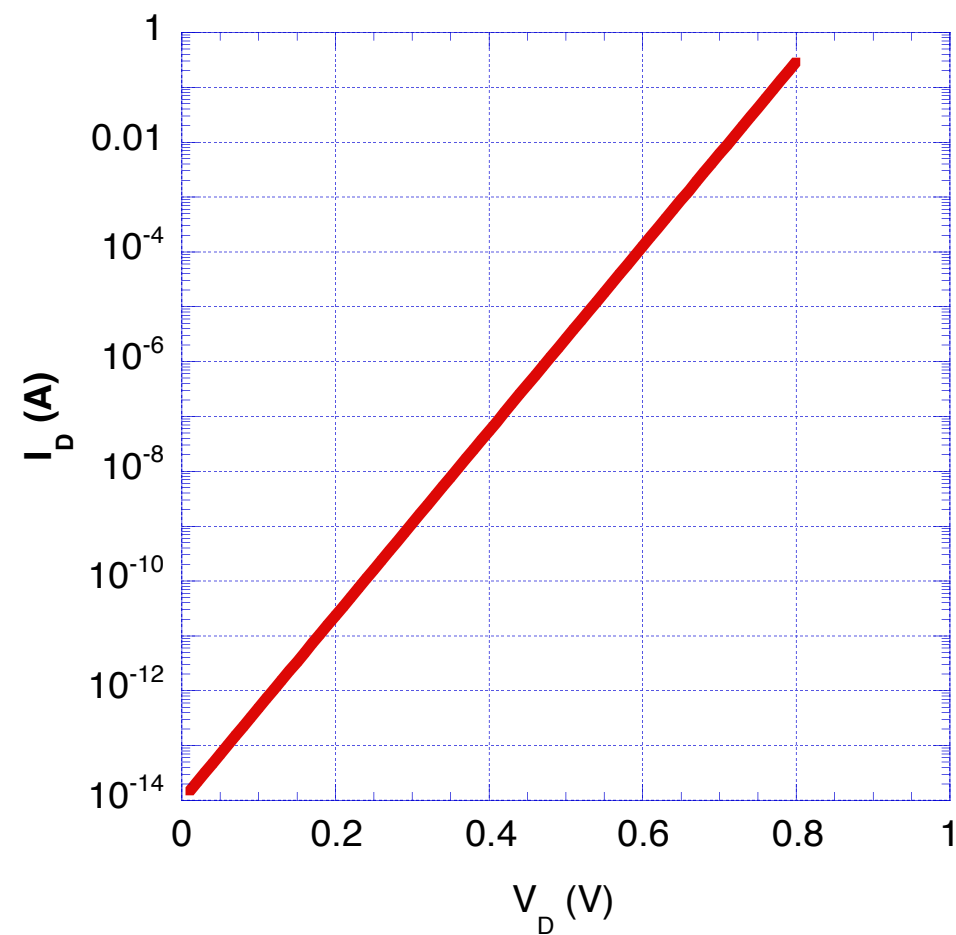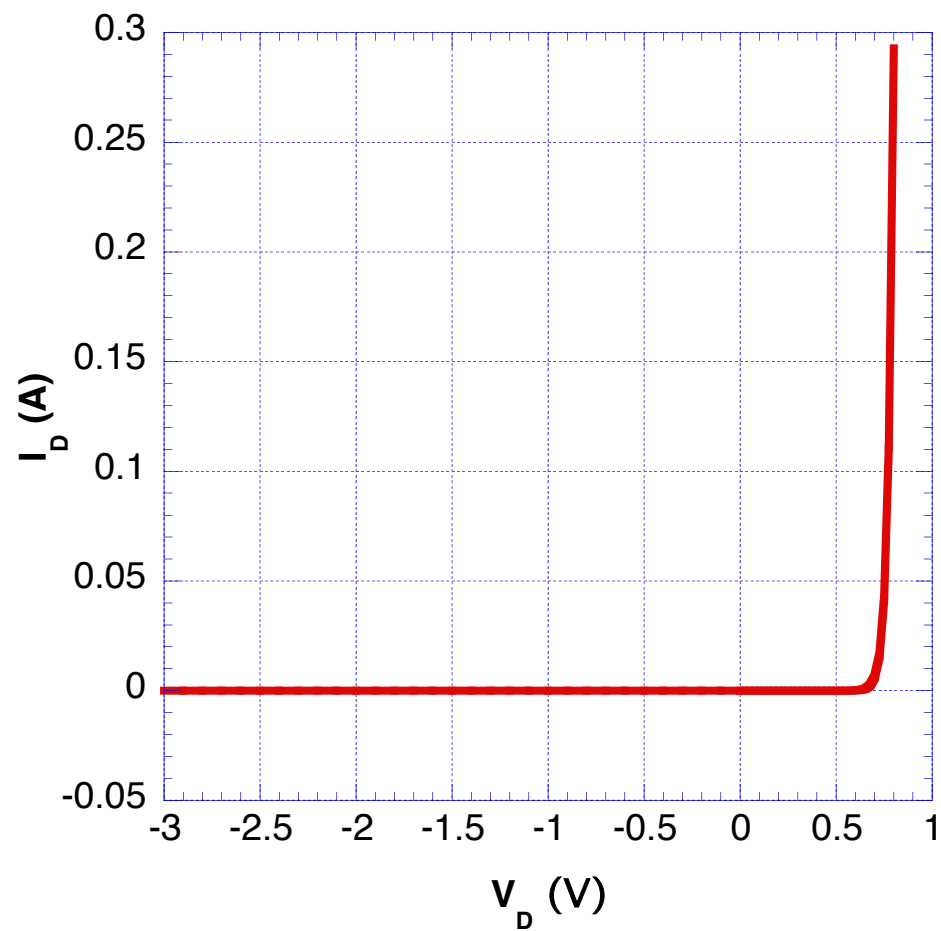The asymmetry between forward and reverse conduction is the basis for rectification – current can flow only one way (essentially). (Again, think funnel.)



Diode i - v
 $I_S = 10^{-14}$ A
 $T = 300$ K

Same diode
 Forward voltage only
 semi-log plot

diodes in circuit

The non-linear behavior has some significant effects.

Basic notions are still valid: KCL and KCL, energy and power

Some techniques are invalid with non-linear elements: superposition, Thevenin.


Node-voltage and mesh-current techniques are still applicable, but the result is a set of non-linear equations, which are difficult to solve.

With non-linear elements, we will rely on:

- Approximating the device behavior with linear elements. This requires some guessing and then checking of the results. Of course, it is only approximate.
- SPICE

diodes in circuits

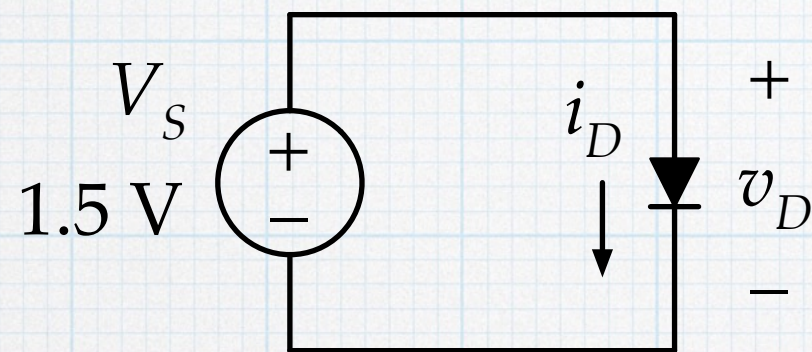Important: When working with diodes, don't EVER apply a forward voltage directly across the diode. The result is usually a dead diode.



$$I_S = 10^{-14} \text{ A}$$


$$\text{room temp: } kT/q = 25.8 \text{ mV.}$$

$$v_D = V_S$$

$$i_D \approx I_S \exp\left(\frac{v_D}{kT/q}\right)$$

$$= \left(10^{-14} \text{ A}\right) \exp\left(\frac{1.5\text{V}}{0.0258\text{V}}\right) = 1.8 \times 10^{+12} \text{ A}$$

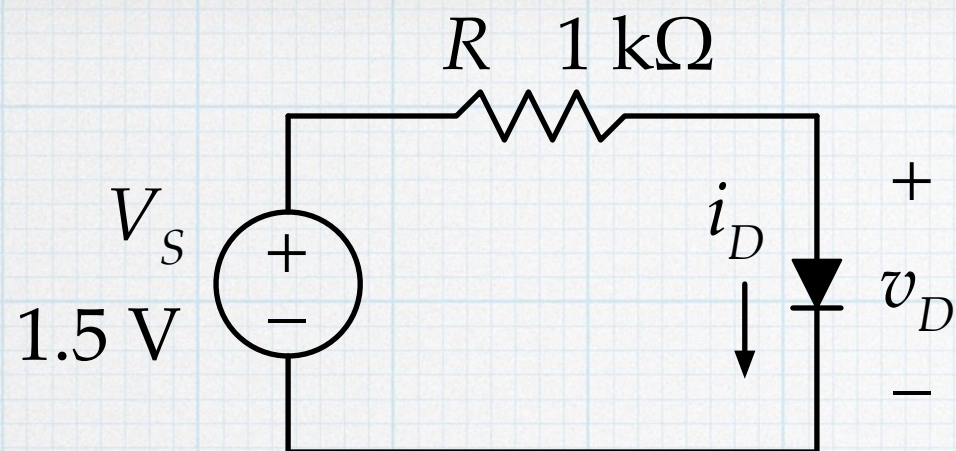This is absolutely absurd. Of course, what really happens is that the diode would burn up (due to instant heating) when the current hits 1 A or so. There must always be a current-limiting resistor in series.



$$I_S = 10^{-14} \text{ A}$$

$$\text{room temp: } kT/q = 25.8 \text{ mV.}$$

$$i_D = I_S \left[\exp \left(\frac{v_D}{kT/q} \right) - 1 \right]$$

$$v_D = \frac{kT}{q} \ln \left(\frac{i_D}{I_S} + 1 \right)$$

$$V_S = v_R + v_D$$

$$V_S = i_D R + \frac{kT}{q} \ln \left(\frac{i_D}{I_S} + 1 \right)$$

??? Can't be solved in closed form.
Transcendental equation. Must use
iteration. (Trial-and-error.)


$$i_D = \frac{V_S}{R} - \frac{kT/q}{R} \ln \left(\frac{i_D}{I_S} + 1 \right) = 1.5 \text{ mA} - (0.0258 \text{ mA}) \ln \left(\frac{i_D}{10^{-11} \text{ mA}} + 1 \right)$$

1st guess

| |
|-------------|
| 1.00 mA |
| 0.846526 mA |
| 0.850825 mA |
| 0.850694 mA |
| 0.850698 mA |

$$i_D = 0.851 \text{ mA}$$

$$v_D = 0.649 \text{ V}$$

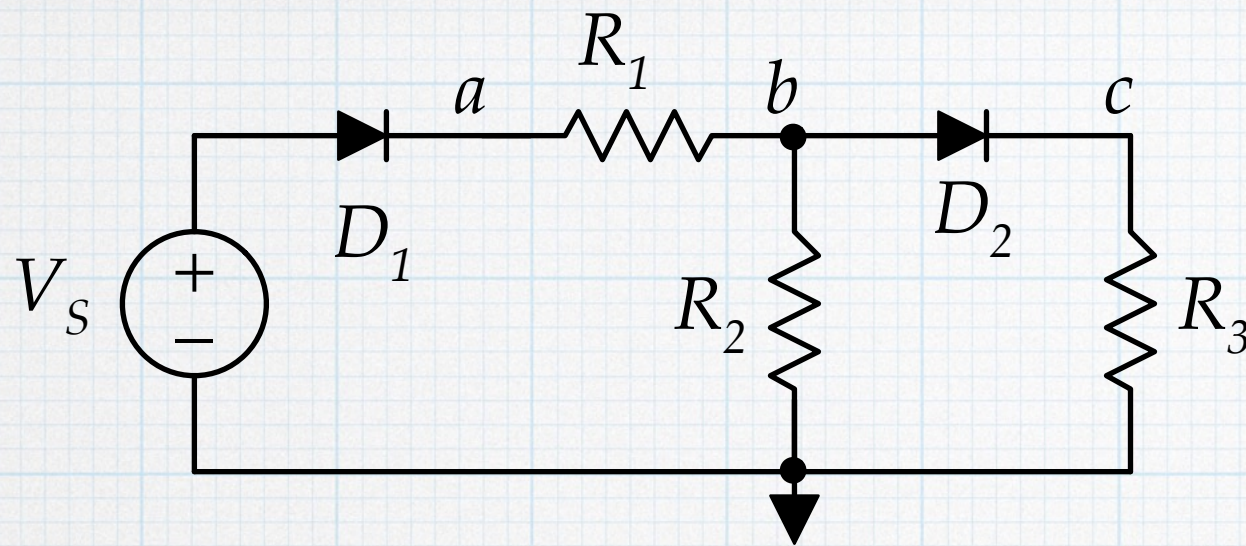

$$i_{D1} = \frac{v_a - v_b}{R_1}$$

$$v_{D1} = V_S - v_a$$

$$\frac{v_a - v_b}{R_1} = \frac{v_b}{R_2} + i_{D2}$$

$$v_{D2} = v_b - v_c$$


$$i_{D2} = \frac{v_c}{R_3}$$

$$I_{S1} \left[\exp \left(\frac{V_S - v_a}{kT/q} \right) + 1 \right] = \frac{v_a - v_b}{R_1}$$

$$\frac{v_a - v_b}{R_1} = \frac{v_b}{R_2} + I_{S2} \left[\exp \left(\frac{v_b - v_c}{kT/q} \right) + 1 \right]$$

$$I_{S2} \left[\exp \left(\frac{v_b - v_c}{kT/q} \right) + 1 \right] = \frac{v_c}{R_3}$$

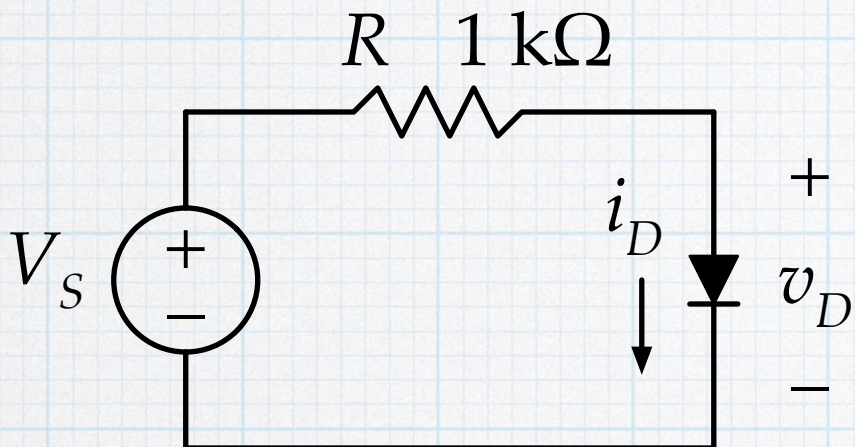3 non-linear equations in 3 unknowns
Good luck with that!!



$$i_D = \frac{V_S}{R} - \frac{kT/q}{R} \ln \left(\frac{i_D}{I_S} + 1 \right)$$

When the diode is reverse-biased ($V_S < 0$, so $v_D < 0$), the diode behaves essentially like an open circuit, $i_D \approx 0$.

When the diode is forward-biased ($V_S > 0$, so $v_D > 0$), the diode voltage is roughly constant at 0.6 V - 0.7 V.


| V_S (V) | v_D (V) | i_D (mA) |
|-----------|-----------|-------------|
| -10 | -10 V | ≈ 0 |
| -8 | -8 V | ≈ 0 |
| -6 | -6 V | ≈ 0 |
| -4 | -4 V | ≈ 0 |
| -2 | -2 V | ≈ 0 |
| 0 | 0 | 0 |
| 1 | 0.628 | 0.372 |
| 2 | 0.661 | 1.339 |
| 3 | 0.6752 | 2.3248 |
| 4 | 0.6844 | 3.3156 |
| 5 | 0.6911 | 4.3088 |
| 6 | 0.6965 | 5.3035 |
| 7 | 0.701 | 6.299 |
| 8 | 0.7047 | 7.2953 |
| 9 | 0.708 | 8.292 |
| 10 | 0.711 | 9.289 |

piecewise diode model


The results of the previous slide suggest the following approximate model.

- When the diode is reverse-biased, we can treat it as if it is an open-circuit
- When the diode is forward-biased, we treat it like an ideal source with a value of 0.7 V.

Reverse ($v_D < 0$)

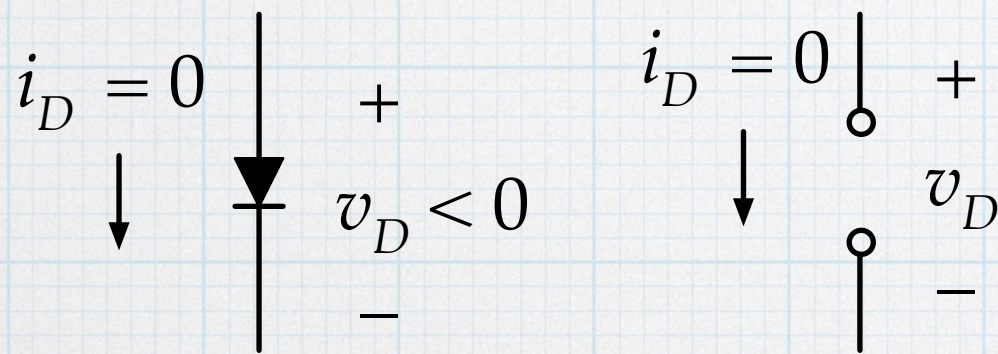


Forward ($v_D > 0$)

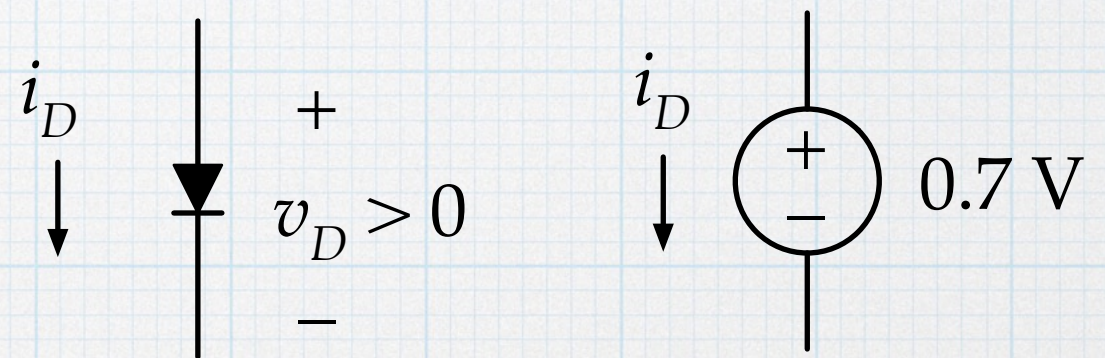


To use the models.

- Guess forward or reverse
- Insert the corresponding model
- Solve for voltage/current using model
- Check the result: for reverse, $v_D < 0$, for forward, i_D flows in correct direction

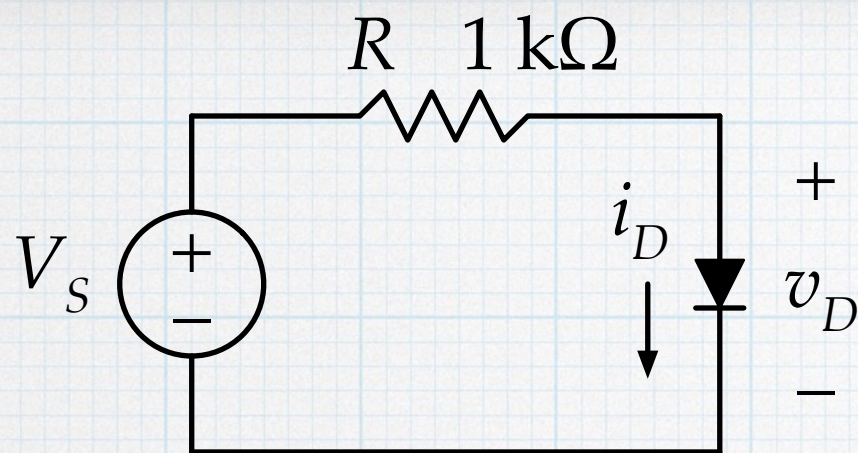
Note that the diode is NOT a voltage source. It does not provide power to the circuit. It simply behaves as if it were a small voltage source or battery that is absorbing power.



Reverse ($v_D < 0$ when $V_S < 0$)

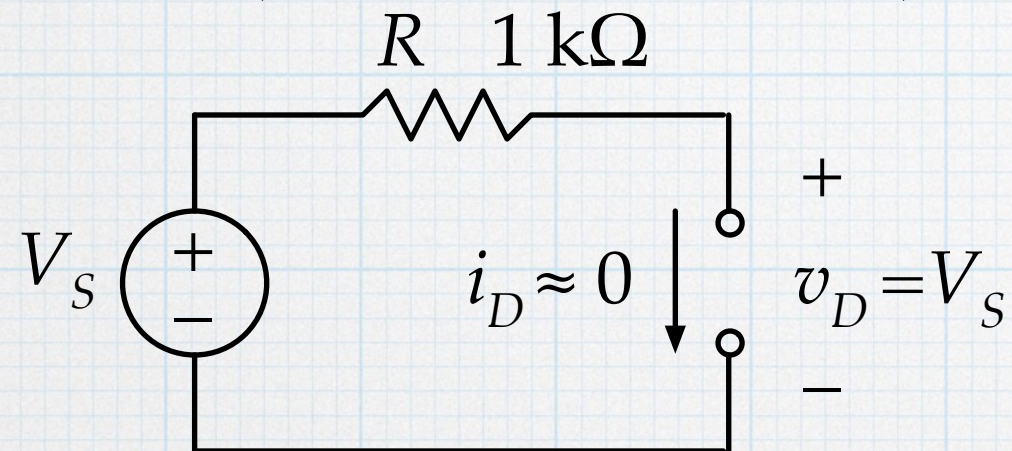

Forward ($v_D > 0$ when $V_S > 0$)

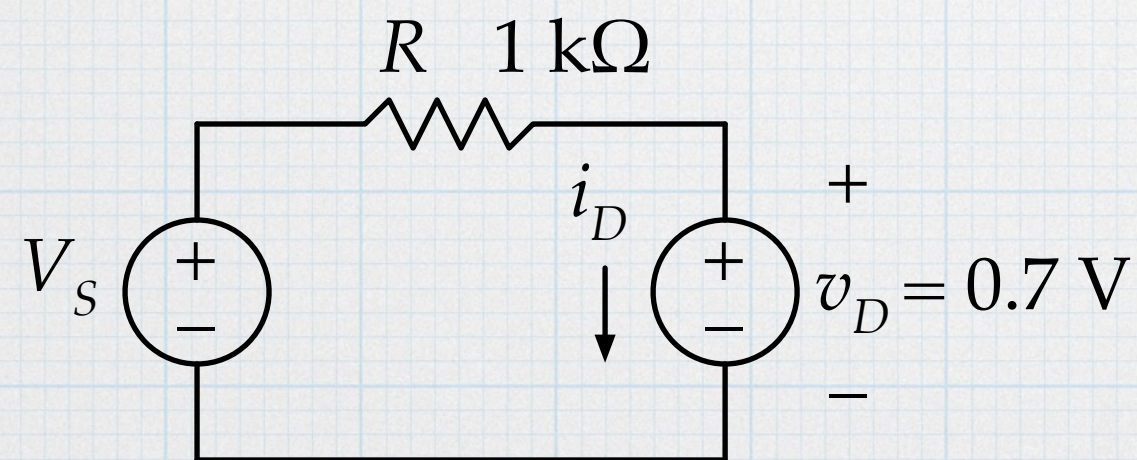


$$i_D = \frac{V_S - v_D}{R} = \frac{V_S - 0.7V}{R}$$

| V_S (V) | v_D (V) | i_D (mA) |
|-----------|-----------|-------------|
| -10 | -10 V | ≈ 0 |
| -8 | -8 V | ≈ 0 |
| -6 | -6 V | ≈ 0 |
| -4 | -4 V | ≈ 0 |
| -2 | -2 V | ≈ 0 |
| 0 | 0 | 0 |
| 1 | 0.7 | 0.3 |
| 2 | 0.7 | 1.3 |
| 3 | 0.7 | 2.3 |
| 4 | 0.7 | 3.3 |
| 5 | 0.7 | 4.3 |
| 6 | 0.7 | 5.3 |
| 7 | 0.7 | 6.3 |
| 8 | 0.7 | 7.3 |
| 9 | 0.7 | 8.3 |
| 10 | 0.7 | 9.3 |

compare to slide 12 – very similar

Example

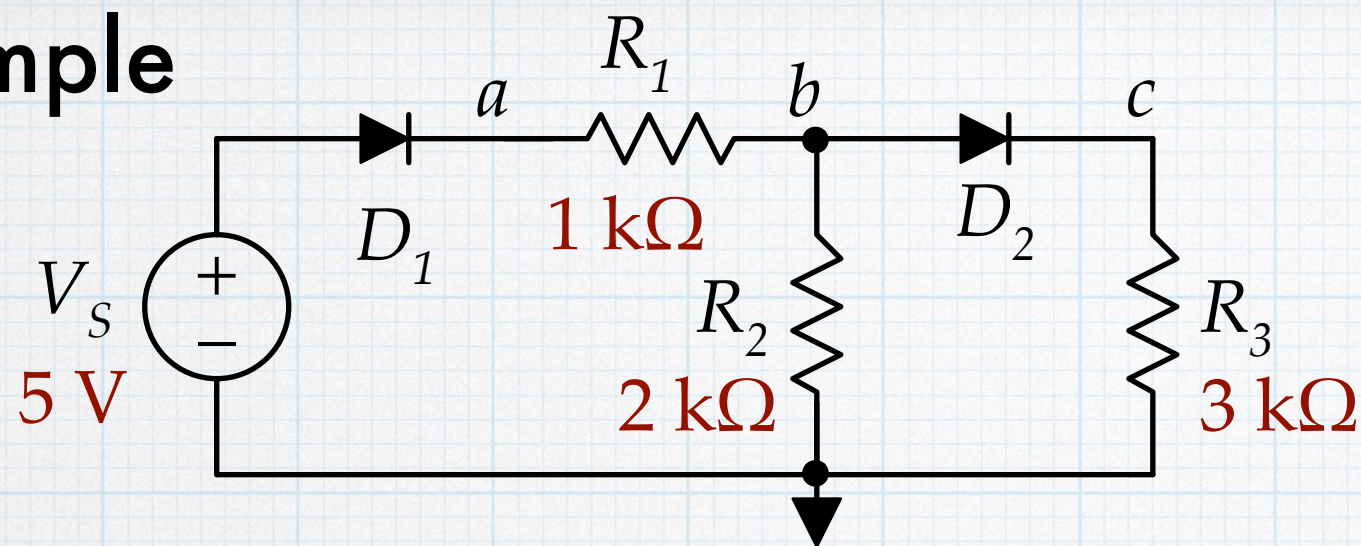

Since V_S is positive, we might guess that both diodes are forward-biased.

$$v_a = V_S - 0.7 \text{ V} = 4.3 \text{ V}.$$


$$v_c = v_b - 0.7 \text{ V}.$$

$$\frac{v_a - v_b}{R_1} = \frac{v_b}{R_2} + i_{D2}$$

$$i_{D2} = \frac{v_c}{R_3} = \frac{v_b - 0.7 \text{ V}}{R_3}$$

$$\frac{V_S - 0.7 \text{ V} - v_b}{R_1} = \frac{v_b}{R_2} + \frac{v_b - 0.7 \text{ V}}{R_3}$$

$$v_b = 2.47 \text{ V}.$$

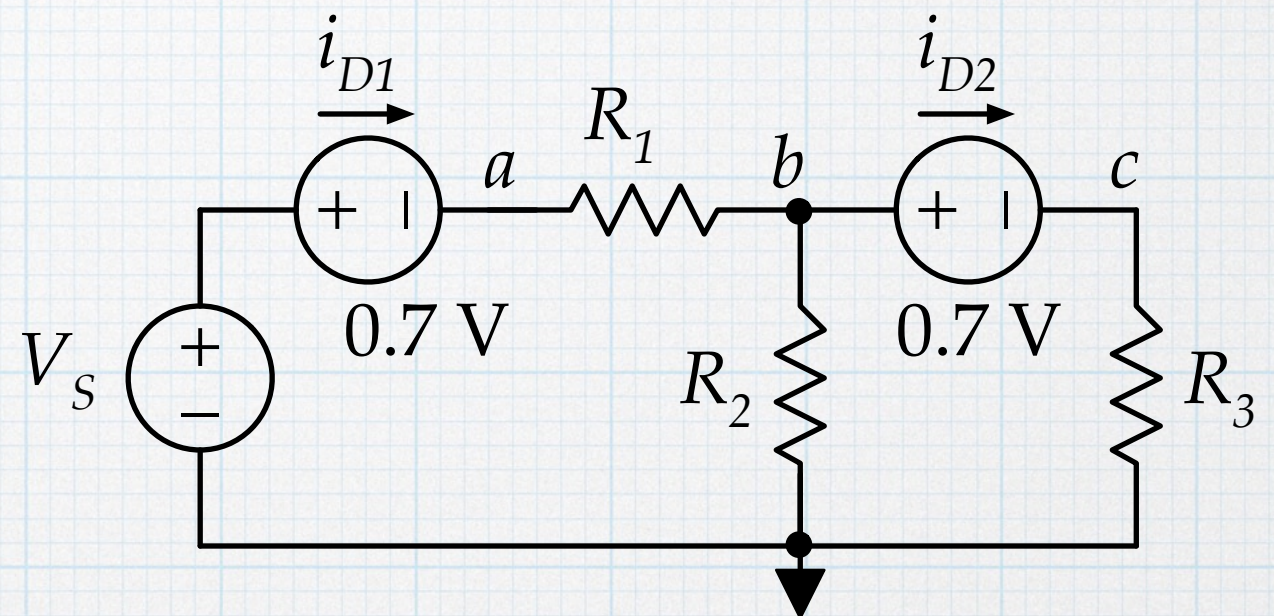

check:

$$i_{D1} = \frac{v_a - v_b}{R_1} = \frac{V_S - 0.7 \text{ V} - v_b}{R_1} = 1.83 \text{ mA}$$

$$i_{D2} = \frac{v_c}{R_3} = \frac{v_b - 0.7 \text{ V}}{R_3} = 0.591 \text{ mA}$$

Both currents are positive, consistent with forward conducting diodes. The guesses were correct.