

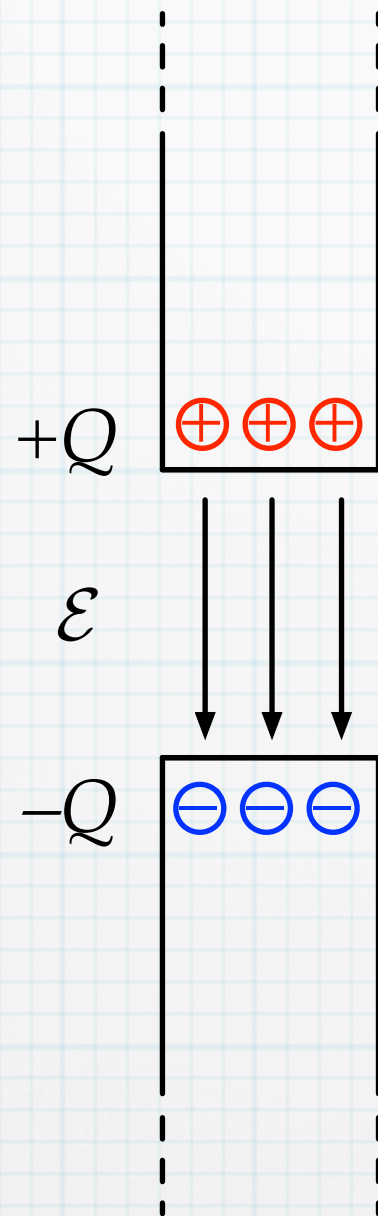


Capacitors

Consider an open circuit:

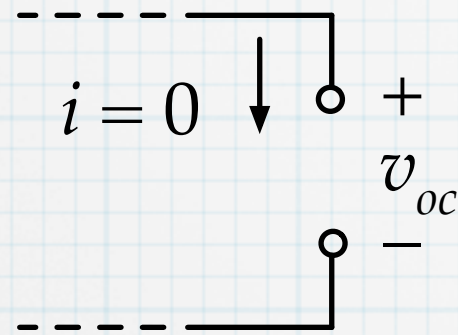

double the voltage

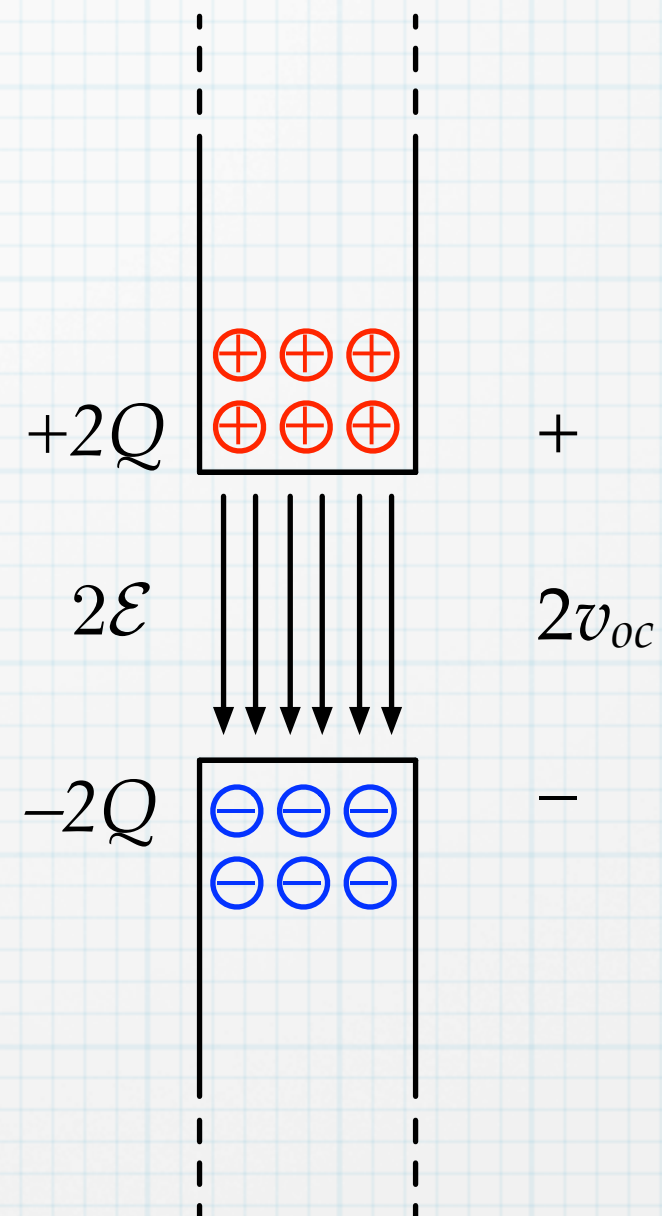

$$Q \propto v_{oc}$$

$$\mathcal{E} \propto v_{oc}$$


There is some energy “stored”.

There was a bit of current flow when the voltage changed.

Effect is weak for dangling wires.
(But not zero!)

Capacitance

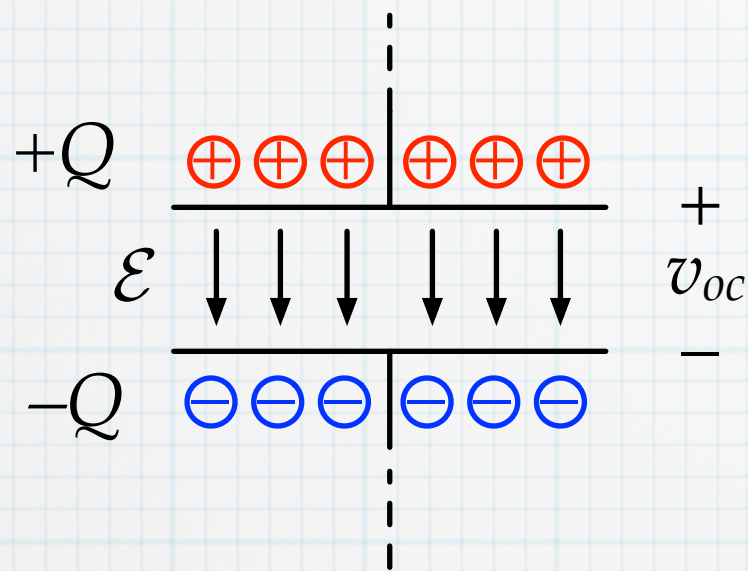Change the geometry – have parallel plates with area A



$$Q = CV$$

$C \rightarrow$ capacitance

farads (F) = C / V

same voltage

- much more charge
- much more electric field
- much more energy stored

$$Q = \epsilon \mathcal{E} A$$

increase charge
with better
dielectric material
and more area.

$$\mathcal{E} = \frac{V}{d}$$


increase field (and
hence Q) by moving
plates closer together

air: $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$

other materials: $\epsilon = \epsilon_r \epsilon_0$

relative dielectric: $\epsilon_r = \text{constant}$

Parallel-plate capacitor

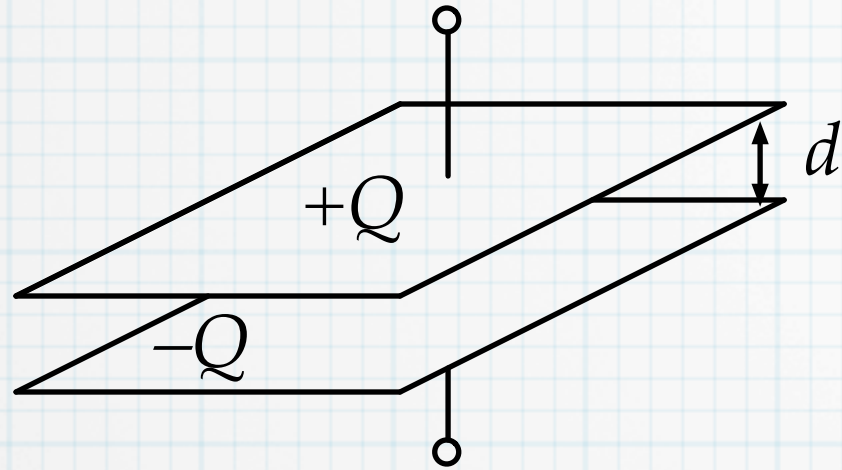

2 plates, each with area A .

$$C = \frac{\epsilon A}{d}$$

Example: $A = 1 \text{ cm}^2$, $d = 0.001 \text{ cm}$, air dielectric

$$C = \frac{(8.8 \times 10^{-14} \text{ F/cm}) (1 \text{ cm}^2)}{0.001 \text{ cm}} = 8.85 \times 10^{-11} \text{ F} = 88.5 \text{ pF}$$

Wow. Very small value, and it is already a fairly large area plate.


Higher values?

- higher dielectric material between the electrodes
- thinner dielectric
- winding or stacking to get larger surface area into a smaller volume.

Other configurations are possible, but parallel-plate is most common.

Values range from 10 pF to 100 μF , (and higher). A 1-F capacitor is huge and quite rare.

Capacitor current

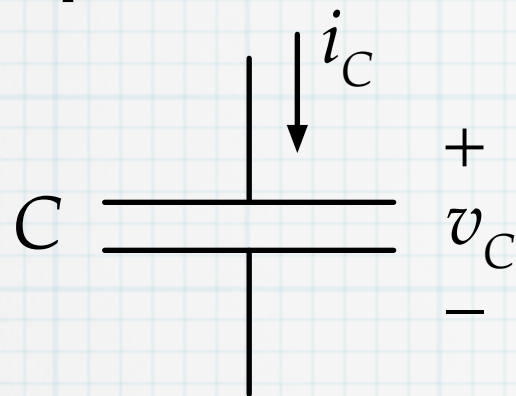

Note that passive sign convention.


At DC, $i_c = 0$. (It's just a fancy open circuit.)

However, some current must flow when voltage is *changing*. Otherwise, the charge would not change.

$$Q = Cv_C$$

$$\frac{dQ}{dt} = i_C = C \frac{dv_C}{dt}$$

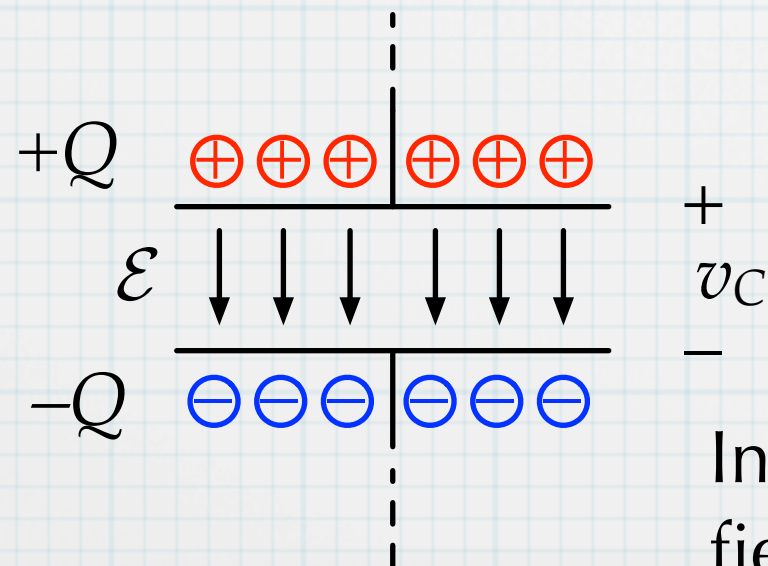Current only flows when voltage is changing.
As current flows, the capacitor charge increases or decreases.




$$\frac{dv_C}{dt} \rightarrow \frac{d\mathcal{E}}{dt} \quad \frac{d\mathcal{E}}{dt} \rightarrow \frac{dQ}{dt}$$

In Maxwell's equations, the current due to changing field is called *displacement* current.

$$i_C = C \frac{dv_C}{dt}$$

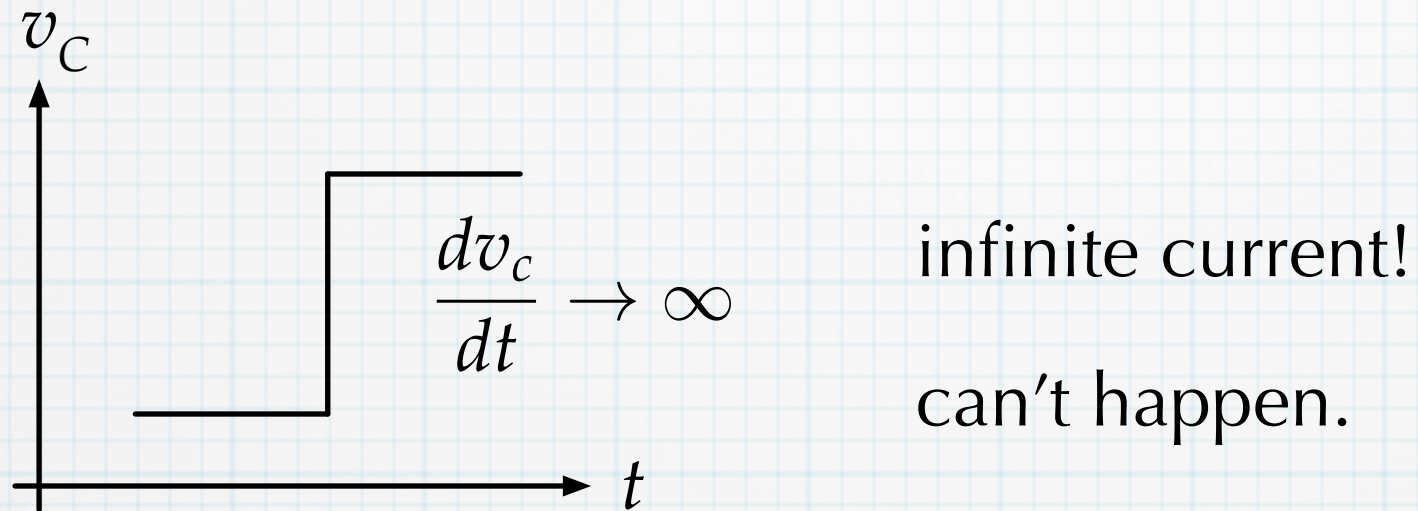Capacitor voltage cannot change instantaneously.



Note, though, that current can change instantaneously.

also

$$v_C(t) = \frac{1}{C} \int_0^t i_C(t') dt' + v_C(0)$$

Capacitor energy

An energy storage device

- Charge the cap to some voltage. Charge (and energy) stays. Remove it later.
- Ideal capacitor dissipates no energy – no heat generated.
- Real capacitors do show some leakage. (Large resistor in parallel.) Usually negligible.

When charging a capacitor, the power being delivered is given by:

$$P_C(t) = v_C(t) i_C(t) = C v_C \frac{dv_C}{dt}$$

The energy delivered by the source, and hence the energy stored in the capacitor is (assuming $v_C = 0$ at $t = 0$ and $v_C(t_f) = V_C$.)


$$P_C(t) dt = C v_C dv_C$$

$$E = \int_0^{t_f} P_C(t) dt = C \int_0^{V_C} v_C dv_C$$

$$E = \frac{1}{2} C V_C^2$$

Combinations of capacitors


Parallel

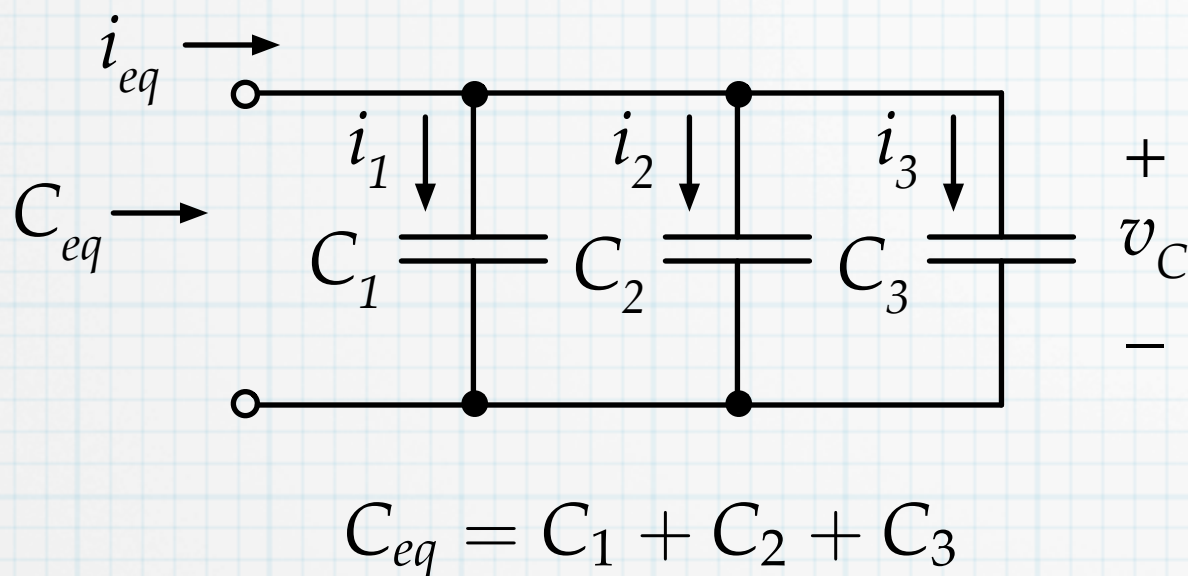

$$i_{eq} = i_1 + i_2 + i_3$$

$$C_{eq} \frac{dv_C}{dt} = C_1 \frac{dv_C}{dt} + C_2 \frac{dv_C}{dt} + C_3 \frac{dv_C}{dt}$$

Series

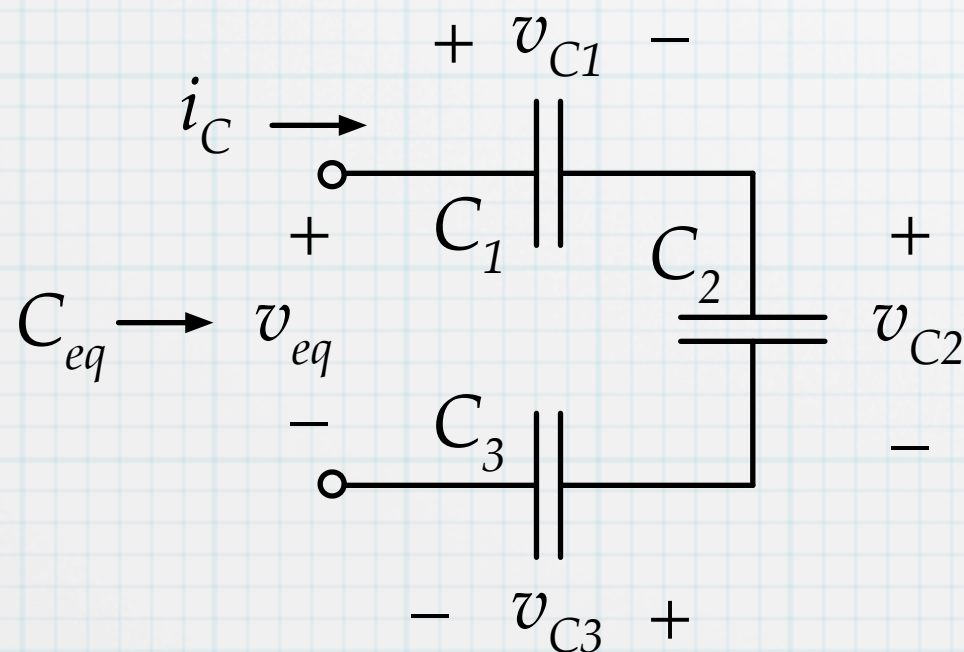

$$v_{eq} = v_{C1} + v_{C2} + v_{C3}$$

$$\frac{dv_{eq}}{dt} = \frac{dv_{C1}}{dt} + \frac{dv_{C2}}{dt} + \frac{dv_{C3}}{dt}$$

$$\frac{i_C}{C_{eq}} = \frac{i_C}{C_1} + \frac{i_C}{C_2} + \frac{i_C}{C_3}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

Capacitors combinations are exactly opposite those of resistors.